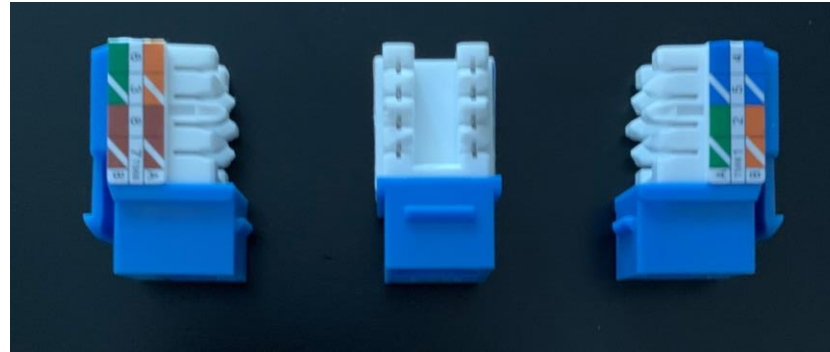


Logix Home PCB

Orange = SENSOR1
Orange/White (GRND)
Brown = SENSOR2
Brown/White (GRND)



Blue = SENSOR3
Blue/White (GRND)
Green = SENSOR4
Green/White (GRND)

When I was confronted with a hoard of wire sticking out the wall where the alarm panel used to exist, it was a task itself to determine which wires went to which sensors. In my case there were 12 zones broken down as follows:



4 doors (front/back/garage entry/basement)

8 windows (living room/dining room/kitchen/bath/family room/basement/basement side)



I would note some of the windows were in pairs and had their own sensors but counted as 1 zone per pair)

I used Network RJ45 connectors to connect the wire pairs to. Each cable that was prewired had 4 wires (red/black/green/yellow)

10K resistor

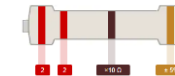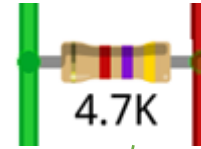

Resistor value:
220 Ohms 5%

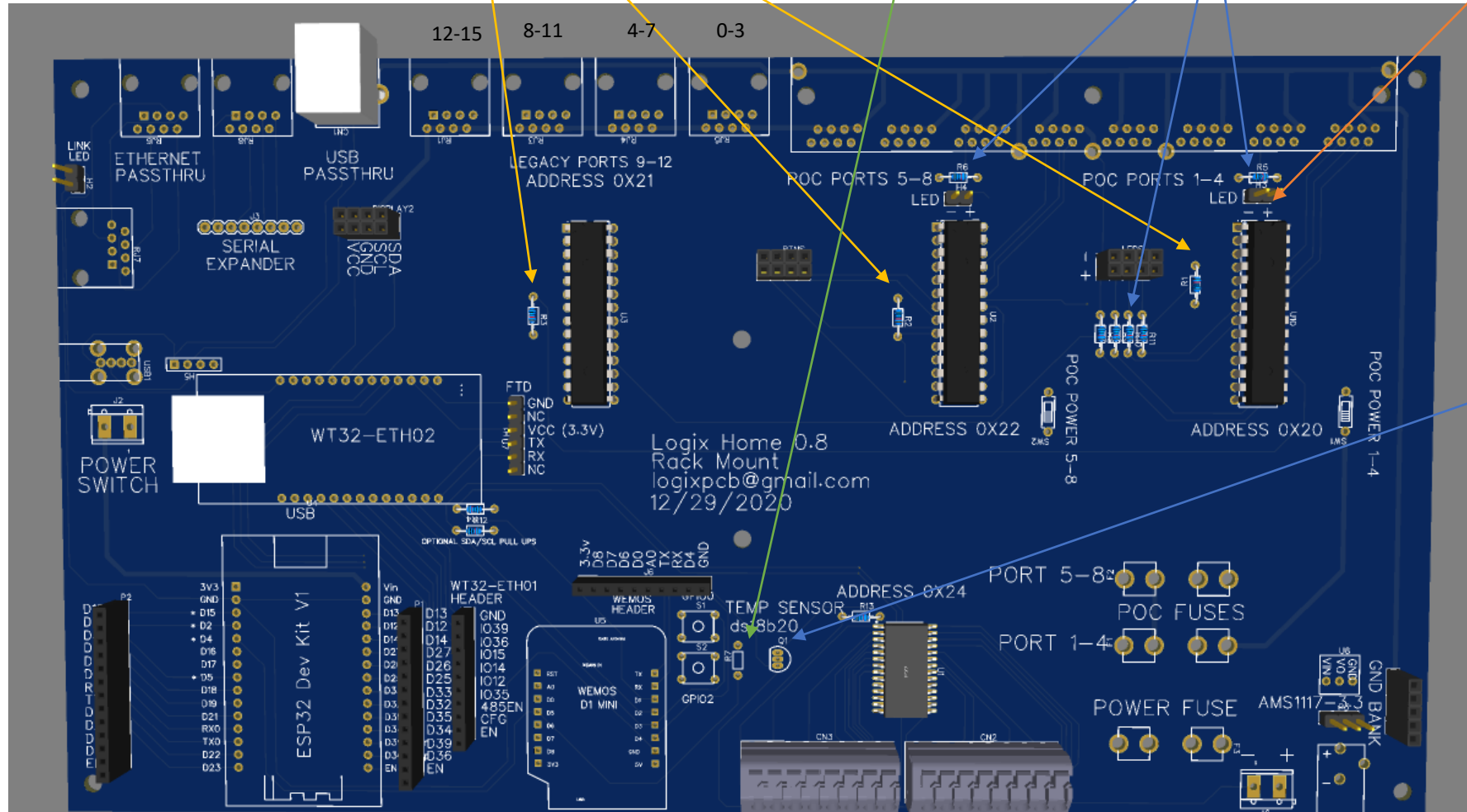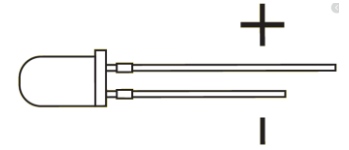

D5 (GPIO14)
ds18b20
*reverse of diagram

8 ports with 3 binary sensors on each (each RJ45 port has 2 pins research for +5v/GGRND)
24 total GPIO

This is a header to connect 4 LED to 4 GPIO on 0x20

This is ahead to connect 4 buttons to 4 GPIO on 0x22

4 ports with 4 binary sensors on each (each twisted pair goes to a GPIO Pin and GRND)
*16 total GPIO

USB passthru (in case you want all the ports in front)

Can also add ethernet passthru if you have an ESP32 with ethernet

5v input

Power switches for POC

Main Fuse (both POC are fused as well)

16 GPIO pins (run any to ground to activate)

Dallas Temp Sensor on D5 of wemos

For Wemos

For ESP32

Connect power switch here

I2C connector for connecting an OLED and such

